

VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI-

590 018



**A MICRO PROJECT REPORT ON
“Overvoltage And Undervoltage Protection System”**

Submitted By,

Mohammed Fahad	4AL20ME015
P R Nisarga	4AL20CS086
Likhita K N	4AL20IS022
Suraj Shrikanth Ankolekar	4AL20IS052

Under the Guidance of

**Mr. Sandeep Kumar
Department of Civil Engineering**



**DEPARTMENT OF BASIC SCIENCES
ALVA'S INSTITUTE OF ENGINEERING AND TECHNOLOGY
MOODBIDRI-574225, KARNATAKA**

2020-2021

ALVA'S INSTITUTE OF ENGINEERING AND TECHNOLOGY

MIJAR, MOODBIDRI D.K. -574225

KARNATAKA




DEPARTMENT OF BASIC SCIENCES

CERTIFICATE

This is to certify that the Micro-Project entitled “**Overvoltage And Undervoltage Protection System**” has been Successfully Completed by

Mohammed Fahad	4AL20ME015
P R Nisarga	4AL20CS086
Likhita K N	4AL20IS022
Suraj Shrikanth Ankolekar	4AL20IS052

The bonafide students of **Department of Basic Sciences, Alva's Institute of Engineering and Technology**, affiliated to **VISVESVARAYA TECHNOLOGICAL UNIVERSITY, BELAGAVI**, during the academic year 2020–2021. It is certified that all corrections/suggestions indicated for Internal Assessment have been incorporated in the report. The report has been approved as it satisfies the academic requirements in respect of Micro-Project work prescribed for Bachelor of Engineering.


Mr. Sandeep Kumar
Mini Project Guide

Dr. Ramaprasad A.T,
HOD Physics
H.O.D.
Dept. Of Physics
Alva's Institute of Engg. & Technology
Mijar, MOODBIDRI - 574 225

ABSTRACT

The goal of this project is to create a system that monitors voltage and provides a low and high voltage tripping mechanism based on breakpoints to protect the load. The AC mains supply fluctuates in a variety of industrial and home systems. There's a danger that electrical gadgets that are sensitive to these changes will be harmed. As a result, a tripping system is required to prevent any damage to these loads. Our system is made up of a tripping mechanism that monitors the input voltage and trips when it reaches certain thresholds. We're using a quad comparator IC with two additional comparators as window comparators. As soon as the input voltage falls outside the window range, the system generates an error. This trigger then activates a relay, which turns off the load to prevent it from being damaged. A lamp is used as a load in this demonstration. In addition, the system is set up with an alarm that sounds when tripping occurs.